

# Digital IC Design

## Lecture 17

### Sequential Circuit Design (1): Latches and Flip-Flops


**Dr. Hesham A. Omran**

Integrated Circuits Laboratory (ICL)  
Electronics and Communications Eng. Dept.  
Faculty of Engineering  
Ain Shams University


This lecture is mainly based on “CMOS VLSI Design”, 4<sup>th</sup> edition, by N. Weste and D. Harris and its accompanying lecture notes
 
# Combinational vs. Sequential Logic

- ❑ Combinational logic circuits
  - Output depends on current inputs
- ❑ Sequential logic circuits
  - Output depends on current and previous inputs
  - Use flip-flops or latches (memory/sequencing elements)
  - Separate previous, current, and next states (tokens)
  - Ex: FSM, pipeline



Finite State Machine

 

Pipeline

# Static vs. Dynamic Logic

- ❑ Combinational logic circuits
  - Static circuits: no clock input
    - e.g., complementary CMOS, pseudo NMOS, and PTL
  - Dynamic circuits: requires clock input
    - e.g., domino logic
- ❑ Sequential logic circuits
  - Static storage: feedback used to retain output indefinitely
  - Dynamic storage: temporary charge on a capacitor
- ❑ Static/dynamic circuits can be sequenced using static/dynamic storage



# Sequencing Elements

## ❑ Latch: Level sensitive

- a.k.a. transparent latch, D latch
- Transparent/opaque
  
## ❑ Flip-flop: edge triggered

- a.k.a. master-slave flip-flop, D flip-flop, D register
- Simply, a pair of latches using clk and its complement
- Edge-triggered






# Sequencing Elements

## ❑ Latch: Level sensitive

- a.k.a. transparent latch, D latch
- Transparent/opaque

   
## ❑ Flip-flop: edge triggered

- a.k.a. master-slave flip-flop, D flip-flop, D register
- Simply, a pair of latches using clk and its complement
- Edge-triggered


 
# Input Timing Constraints






- ❑ Flip-flop samples  $D$  at clock edge
  - $D$  must be stable when sampled
  - Similar to a photograph,  $D$  must be stable around clock edge
  - If not, metastability can occur
- ❑ **Setup time:**  $t_{\text{setup}}$  = time *before* clock edge data must be stable (i.e. not changing)
- ❑ **Hold time:**  $t_{\text{hold}}$  = time *after* clock edge data must be stable
- ❑ **Aperture time:**  $t_a$  = time *around* clock edge data must be stable ( $t_a = t_{\text{setup}} + t_{\text{hold}}$ )



# Timing Diagrams

- ❑ Contamination delay: output may begin to change or glitch
- ❑ Propagation delay: output must have settled to final value

$t_{pd}$	Logic Prop. Delay
$t_{cd}$	Logic Cont. Delay
$t_{pcq}$	Latch/Flop Clk-to-Q Prop. Delay
$t_{ccq}$	Latch/Flop Clk-to-Q Cont. Delay
$t_{pdq}$	Latch D-to-Q Prop. Delay
$t_{cdq}$	Latch D-to-Q Cont. Delay
$t_{setup}$	Latch/Flop Setup Time
$t_{hold}$	Latch/Flop Hold Time
$t_a$	Aperture time

     

# Latch Design

- ❑ Pass Transistor Latch

- ❑ Pros

  - + Tiny

  - + Low clock load

- ❑ Cons

  - $V_t$  drop


  - dynamic (leakage)

  - nonrestoring

  - backdriving

  - output floating (noise sensitivity)

  - diffusion input

 

Used in 1970's



# Latch Design

- ❑ Transmission gate

- ❑ Pros

  - + **No  $V_t$  drop**

  - + Tiny

  - + Low clock load

- ❑ Cons

  - **Requires inverted clock**


  - dynamic (leakage)

  - nonrestoring

  - backdriving


  - output floating (noise sensitivity)

  - diffusion input

 
 
# What is Bad About Diffusion Input?


- ❑ Diffusion input is sensitive to noise
- ❑ Ex: power supply noise and/or coupling noise drove the input voltage below  $-V_t$  relative to GND seen by the transmission gate
  - $V_{gs}$  now exceeds  $V_t$  for the NMOS
  - The transmission gate turns on
- ❑ If the latch stores 1, it could be incorrectly discharged to 0
- ❑ Also makes the delay harder to model with static timing analyzers
  - Delay will be dependent on the level of the input signal strong/weak
- ❑ However, exposing the diffusion input results in a faster latch
  - Can be used in datapaths where the inputs are carefully controlled and checked



# Latch Design

 
## ❑ Inverting buffer

- + Restoring
- + No backdriving
- + Fixes either
  - Output noise sensitivity
  - Or diffusion input
- Inverted output




## ❑ Similar to a clocked tristate inverter: Clocked CMOS ( $C^2$ MOS)

- But TG design is slightly faster

 

 
# Latch Design

- ❑ Dynamic latches are sensitive to leakage
  - Requires min clock frequency (to refresh output)
  - Not compatible with clock gating
  - Leakage is worse in burn-in testing at elevated temperature and voltage
  - Not used in MPUs beyond  $0.35\mu m$
- ❑ Tristate feedback
  - + Static
    - Backdriving risk (Output 'Q' may affect the state node 'X')
- ❑ Static latches are now essential because of leakage
  - But they are larger and slower than dynamic latches



 
# Latch Design

- Buffered input
  - + Fixes diffusion input
  - + Noninverting



 
# Latch Design

- ❑ Buffered output
  - + No backdriving
  
- ❑ **Widely used in standard cells**
  - + Very robust (most important)
  - Rather large
  - Rather slow (1.5 – 2 FO4 delays)
  - High clock loading
  
- ❑ Recommended for all but performance- or area-critical designs


 
# Latch Design


- ❑ In semicustom datapath applications input noise can be better controlled
- ❑ Datapath latch
  - + smaller
  - + faster
    - unbuffered input
- ❑ Intel uses this as a standard datapath latch



# Latch Design

 
## ❑ Jamb latch

- Uses a weak feedback inverter in place of the tristate
- Saves two transistors
- Reduces the clock load
- But requires careful design to ensure that the tristate overpowers the feedback inverter in all corners


 
## ❑ Itanium 2 processor latch

- Pulldown stack is clocked
- Pullup is a weak PMOS transistor





# Flip-Flop Design



❑ Flip-flop is built as pair of back-to-back latches

❑ Dynamic

- Leakage
- Not used in MPUs beyond  $0.35\mu m$


❑ Static

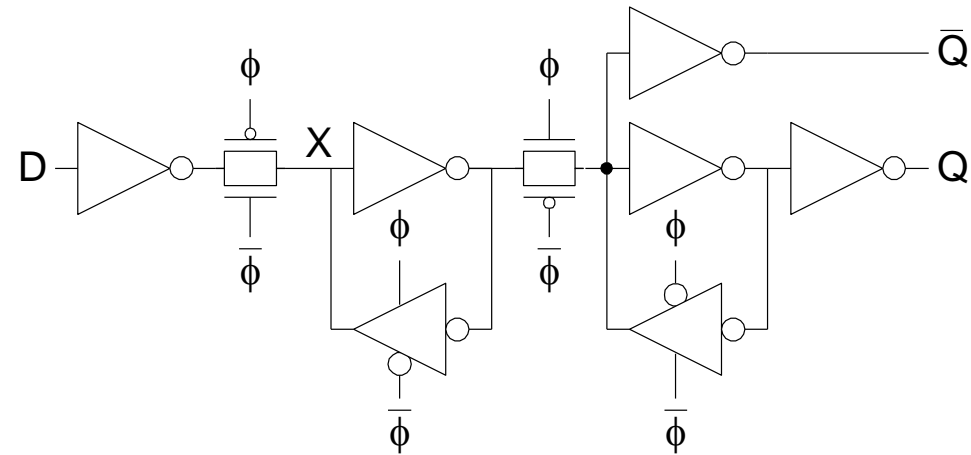 - **Conventional flip-flop widely used in std cells**
- Simple, robust, and energy-efficient
- **But other alternatives may be faster**
- In Artisan library, the clock is buffered and complemented in every flip-flop cell



 
# Flip-Flop Race Condition

- ❑ Skew between  $\Phi$  and  $\bar{\Phi}$ : Both PMOS ON
- ❑ CMOS-TG: both latches are transparent  $\rightarrow$  race condition



 
- ❑ C<sup>2</sup>MOS: skew tolerant (you must go through NMOS and PMOS)
  - But clock must be reasonably sharp to avoid races
  - Even no. of logic stages can be placed between latches: NO RAcE CMOS (NORA)




- ❑ Practically: CMOS-TG is slightly faster and is carefully designed to be safe
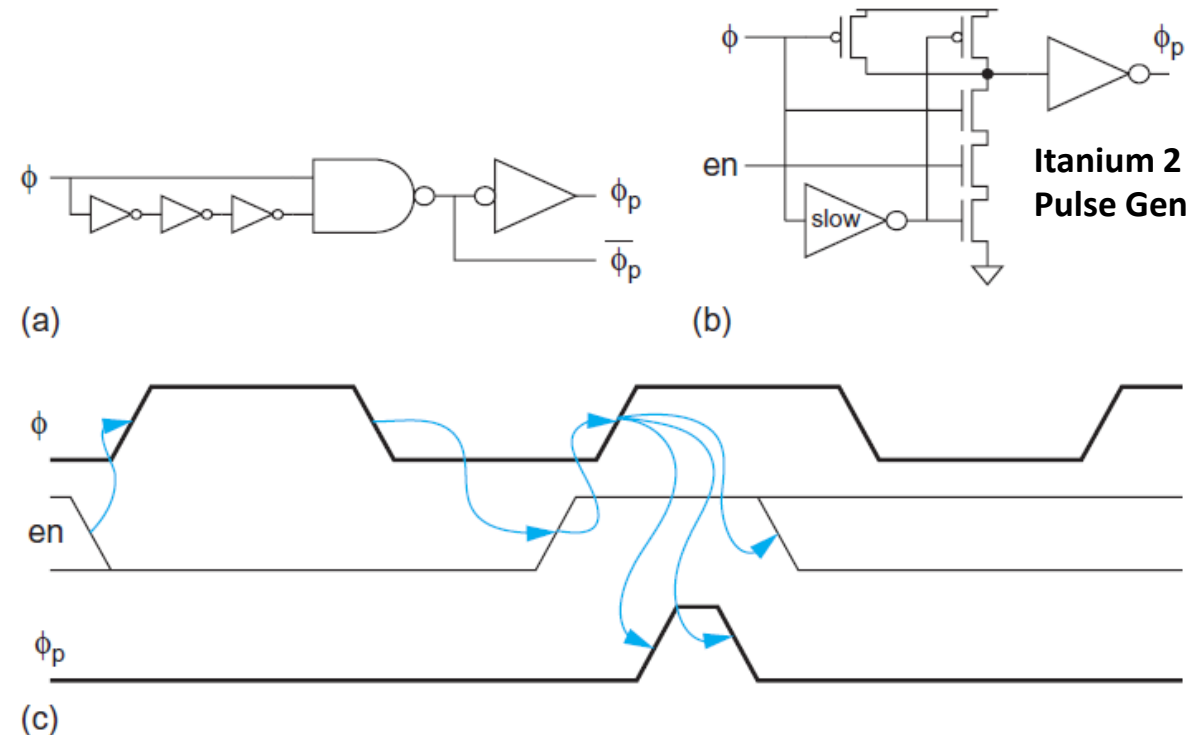
# Pulsed Latch

- ❑ Conventional transparent latch driven by a clock pulse
- ❑ Pulse generator (one-shot) is required
  - Adds to the energy consumption
  - Shared across multiple latches for energy and area efficiency
- ❑ Faster than flip-flop, but increases hold time



# Delay Trade-Offs

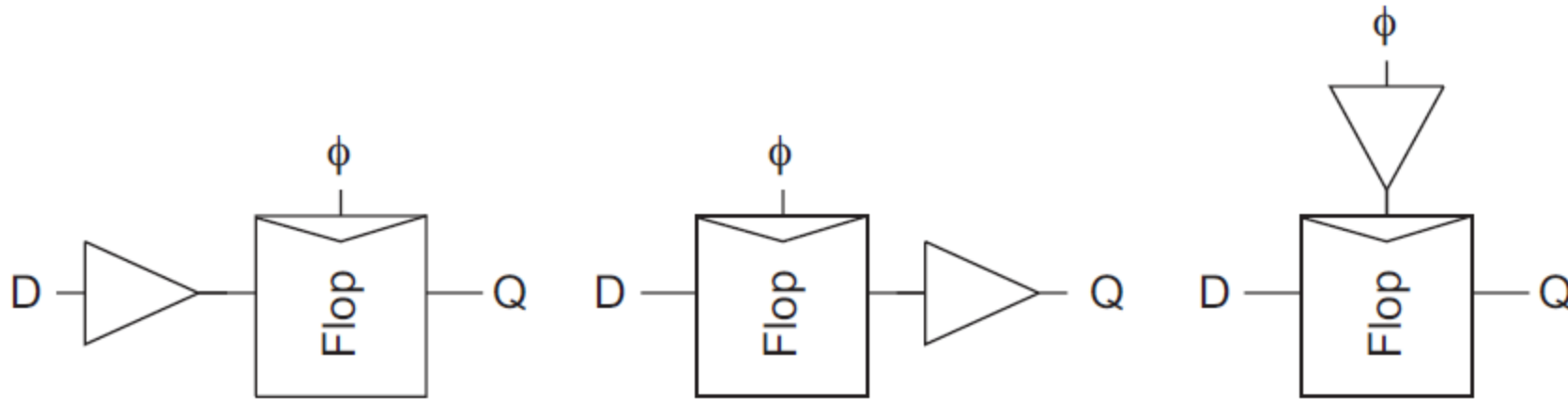


$$t'_{\text{setup}} = t_{\text{setup}} + t_{\text{buf}}$$

$$t'_{pcq} = t_{pcq}$$

$$t'_{\text{hold}} = t_{\text{hold}} - t_{\text{buf}}$$



# Delay Trade-Offs

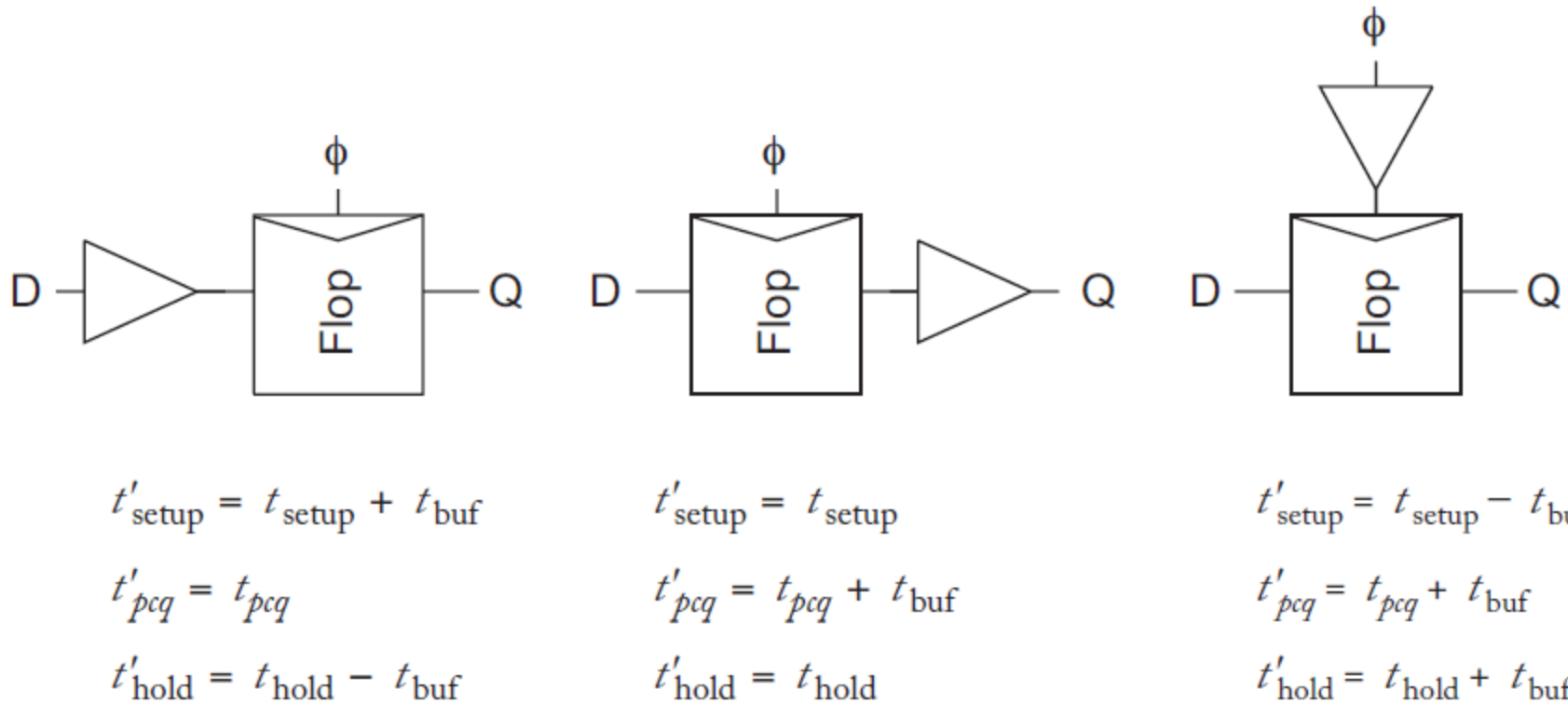



# Reset

- ❑ Force output low when reset asserted
- ❑ Synchronous vs. asynchronous
- ❑ Tristate NAND gate = NAND gate + clocked TG

Synchronous  
Reset

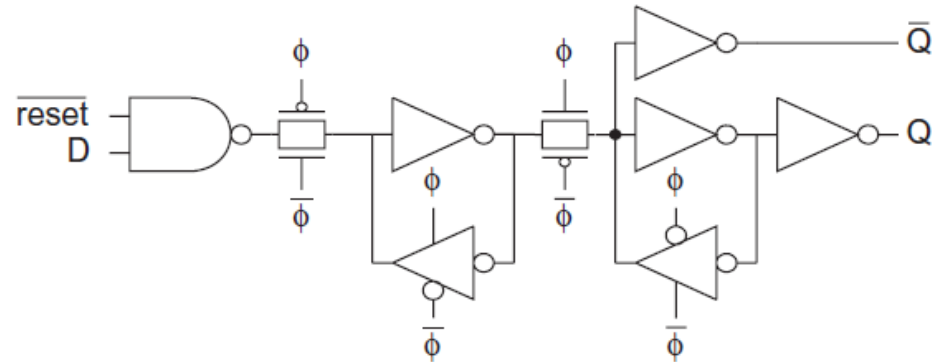 


Asynchronous  
Reset

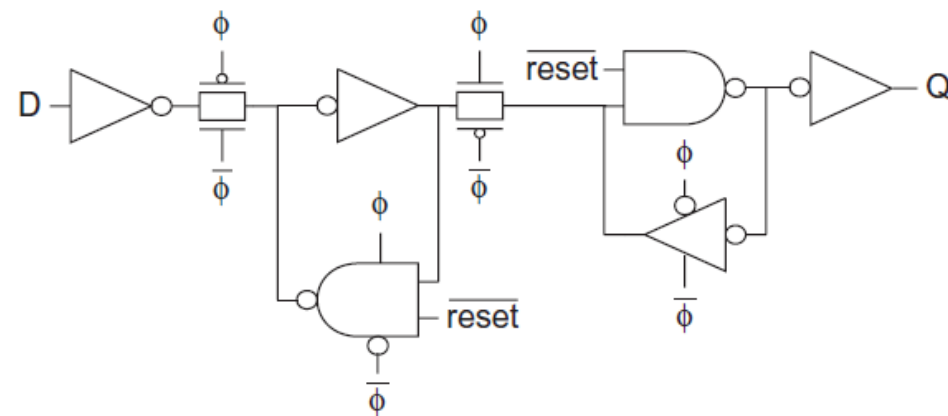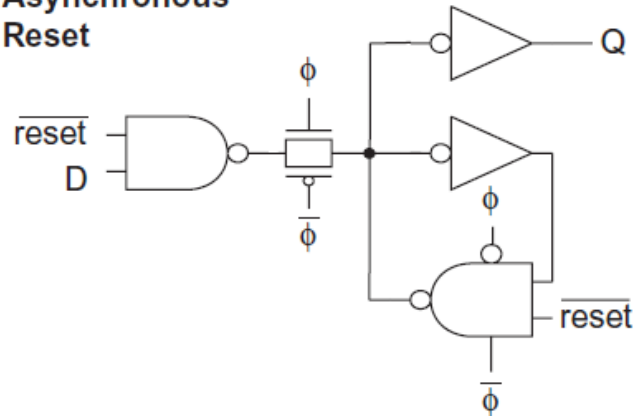
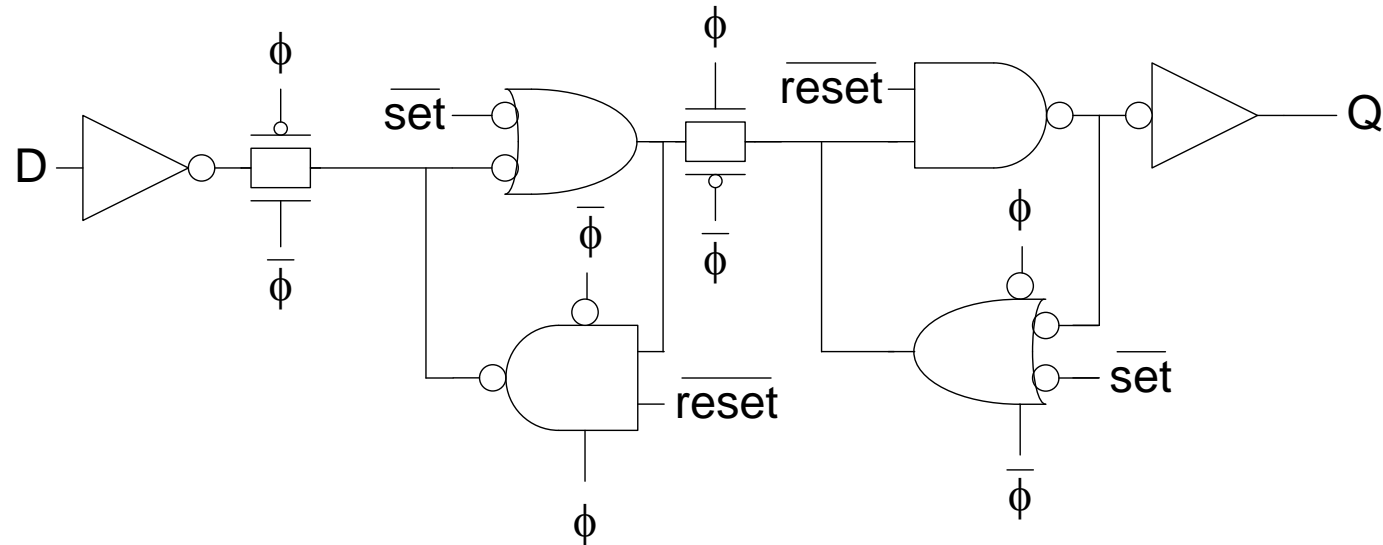
# Set / Reset


- ❑ Set forces output high when enabled
- ❑ Flip-flop with asynchronous set and reset
- ❑ Recovery time: time between removing set/reset to clk input






# Enable

- ❑ Enable: ignore clock when  $en = 0$ 
  - Mux: increases latch D-Q delay, area (safe choice)
  - Clock Gating: saves power, but hazardous, constrains en timing, adds skew

Multiplexer Design

 


Clock Gating Design

   





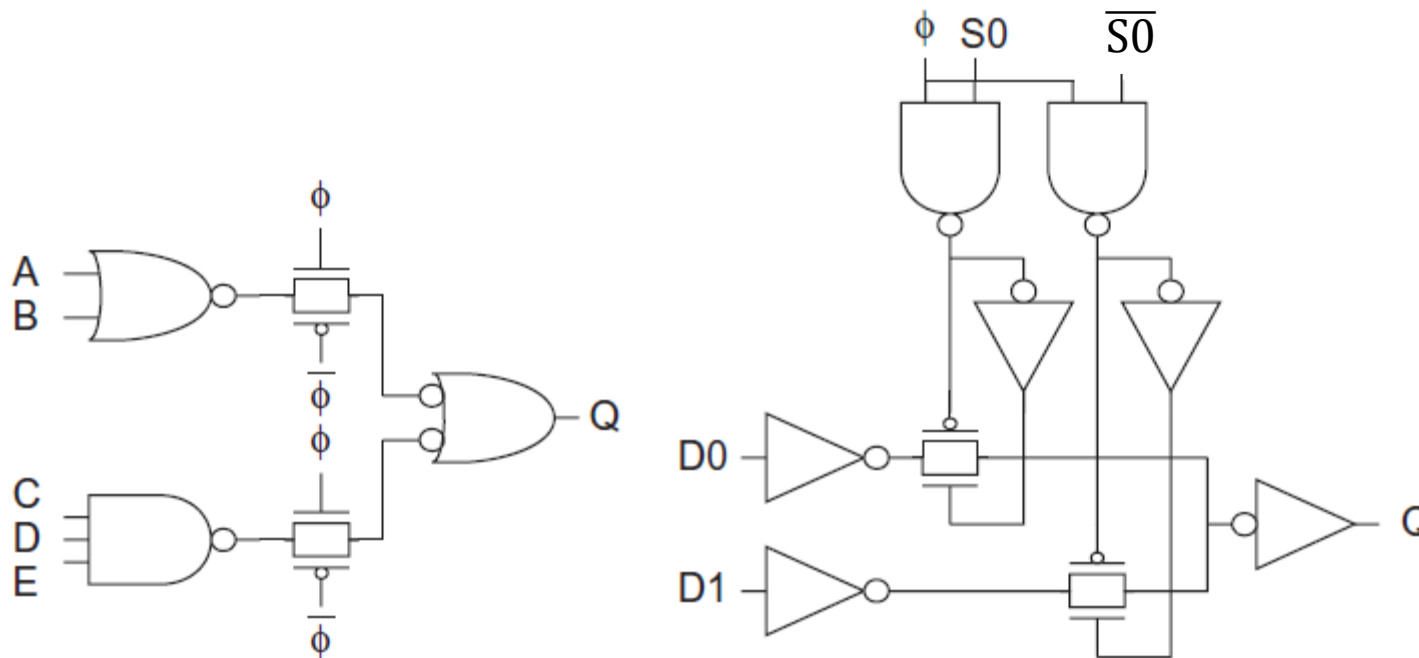
# Logic into Latches

- ❑ Reduce sequencing overhead by incorporating logic into latches
- ❑ Replace inverters with gates that perform useful computation
- ❑ Mux-latch:
  - Integrates the multiplexer function with no extra delay from the D inputs to the Q
  - Setup time on the select inputs is relatively high.



   
# True Single-Phase Clock (TSPC) Latches

- ❑ CMOS-TG or C<sup>2</sup>MOS require  $\Phi$  and  $\bar{\Phi}$
- ❑ TSPC uses  $\Phi$  only
- ❑ TSPC flip-flop produces a momentary low glitch on  $\bar{Q}$  after the rising clock edge when D is low
  - Increases the activity factor of downstream circuits
- ❑ Not easy to staticize
- ❑ Clock must be reasonably sharp to avoid races
- ❑ TSPC is primarily of historical interest
  - But still useful for HS full custom digital, e.g., PLLs and serial links



 
# Differential Sense-Amplifier Flip-Flop

- ❑ Built from a clocked sense amplifier so that it can rapidly respond to small differential input voltage
  - Used in StrongARM MPU in the 1990s (a.k.a. StrongARM latch)
- ❑ CLK = 0: internal nodes  $X$  and  $\bar{X}$  precharge.
- ❑ CLK = 1: one of  $X$  and  $\bar{X}$  is pulled down
- ❑ SR latch: slave stage, captures output and holds it during Precharge (static output)




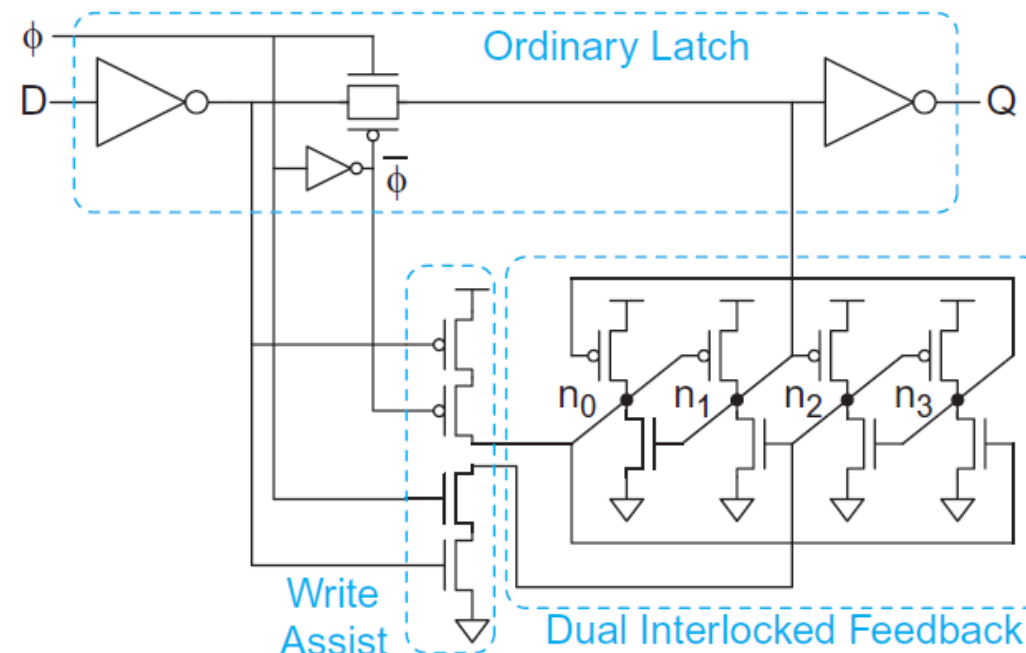
# Radiation-Hardened Flip-Flops

- ❑ Soft errors are random nonrecurring errors triggered by radiation striking a chip (mostly from cosmic radiation)
  - Critically important for space applications
- ❑ Traditionally affected DRAMs, but becoming more important for registers as charge diminishes (scaling dimensions and voltage)
- ❑ If one node ( $n_1$  to  $n_4$ ) is disturbed, the feedback will restore it



 
 
# Characterizing Sequential Circuits

- ❑ Read Section 10.4.2 in the textbook: Characterizing Sequencing Element Delays
- ❑  $t_{DQ}$  is min when the slope of  $t_{CQ}$  is -1 (increase/decrease in  $x$  is counteracted by an equal decrease/increase in  $y$ )


 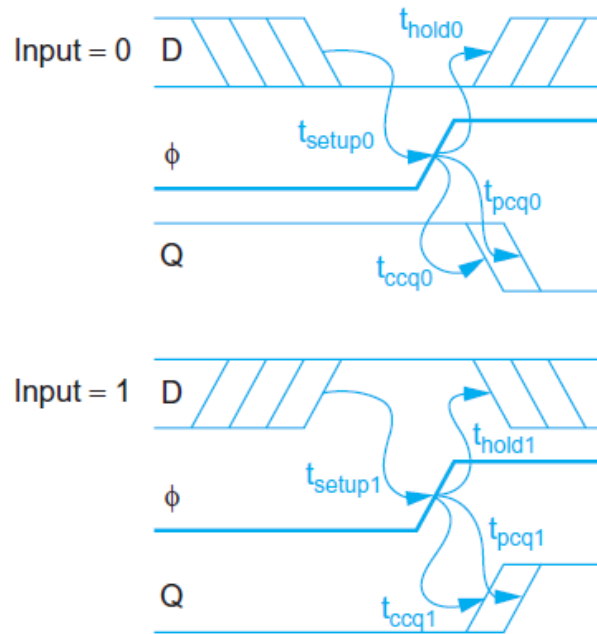
# Characterizing Sequential Circuits

- Aperture time: The time that input must remain '0' or '1' to be correctly sampled



---

**Thank you!**

# Characterizing Sequential Circuits

## ❑ Latch delay vs. data arrival time

